
Internet Connections

- © TryEngineering (www.tryengineering.org)
- © IEEE Virtual Museum (www.ieee-virtual-museum.org)
- © ITEA Standards for Technological Literacy: Content for the Study of Technology (www.iteawww.org/TAA/Publications/STL/STLMainPage.htm)
- © McREL Compendium of Standards and Benchmarks (www.mcrel.org/standards-benchmarks)
A compilation of content standards for K-12 curriculum in both searchable and browsable formats.
- © National Council of Teachers of Mathematics Principals and Standards for School Mathematics (www.nctm.org/standards)
- © National Science Education Standards (www.nsta.org/standards)


Recommended Reading

- © DK Eyewitness Series: Electricity (ISBN: 0751361321)
- © Eyewitness Electricity, by Steve Parker (DK Publishing, ISBN: 0789455773)
- © How Science Works, by Judith Hann (Readers Digest, ISBN: 0762102497)

Optional Writing Activity

- © Write an essay, or a paragraph, describing how switches found on common appliances in the home make those appliances more functional, or easier to operate.

Electric Switches

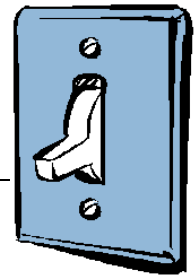

For Teachers: Alignment to Curriculum Frameworks

Note: All lesson plans in this series are aligned to the National Science Education Standards which were produced by the National Research Council and endorsed by the National Science Teachers Association, and if applicable, also to the International Technology Education Association's Standards for Technological Literacy or the National Council of Teachers of Mathematics' Principals and Standards for School Mathematics.

¥ National Science Education Standards Grades K-4 (ages 4 - 9)

CONTENT STANDARD A: Science as Inquiry

As a result of activities, all students should develop

- ⦿ Abilities necessary to do scientific inquiry
- ⦿ Understanding about scientific inquiry

CONTENT STANDARD B: Physical Science

As a result of the activities, all students should develop an understanding of

- ⦿ Light, heat, electricity, and magnetism

CONTENT STANDARD E: Science and Technology

As a result of activities, all students should develop

- ⦿ Understanding about science and technology

¥ National Science Education Standards Grades 5-8 (ages 10 - 14)

CONTENT STANDARD A: Science as Inquiry

As a result of activities, all students should develop

- ⦿ Abilities necessary to do scientific inquiry
- ⦿ Understandings about scientific inquiry

CONTENT STANDARD B: Physical Science

As a result of their activities, all students should develop an understanding of

- ⦿ Transfer of energy

CONTENT STANDARD E: Science and Technology

As a result of activities, all students should develop

- ⦿ Understandings about science and technology

¥ Standards for Technological Literacy - All Ages Design

- ⦿ Standard 8: Students will develop an understanding of the attributes of design.
- ⦿ Standard 9: Students will develop an understanding of engineering design.
- ⦿ Standard 10: Students will develop an understanding of the role of troubleshooting, research and development, invention and innovation, and experimentation in problem solving.

Electric Switches



For Teachers: Teacher Resources

¥ Materials

- Student Worksheet
- One set-up for each group of students, consisting of:
 - Different types of switches
 - Wire
 - Battery Holder
 - D size Battery
 - Socket
 - 1.5 volt bulb
 - Motors
 - Buzzers
 - Paper clips
 - Metal hair clips
 - Aluminum foil
 - Pliers
 - Discarded toys and appliances

¥ Procedure

1. Ask students for examples of how switches are used. Record their responses on chart paper or classroom board.
2. Divide students into small groups or 4 to 5 students.
3. Have students build a working circuit with just a battery and a bulb.
4. Next, ask students to add a switch in such a way that the switch turns the bulb on and off.
5. Have students draw and describe their circuits and switches in the student worksheet using schematic symbols found on the Student Resource Sheet.
6. Bring the student groups together to discuss their designs and experiences.

¥ Time Needed

45 Minutes


¥ Tips

- If students have difficulty in creating a switch, suggest they use a paper clip bent so it can just barely touch a piece of foil or another paper clip when pressed; or a paper fastener wedged in between a battery and battery holder which prevents them from making contact when pressed.

¥ Extension

Have students look for switches in discarded toys, appliances, or other electrical devices. Students can disassemble the items to see how they work.


Electric Switches

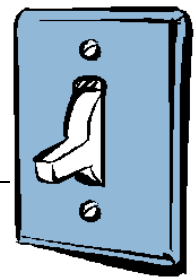

Student Resource: What is a Simple Circuit?

¥ Simple Circuit


A simple circuit consists of three minimum elements that are required to complete a functioning electric circuit: a source of electricity (battery), a path or conductor on which electricity flows (wire) and an electrical resistor (lamp) which is any device that requires electricity to operate. The illustration below shows a simple circuit containing, one battery, two wires, and a bulb. The flow of electricity is from the high potential (+) terminal of the battery through the bulb (lighting it up), and back to the negative (-) terminal, in a continual flow.

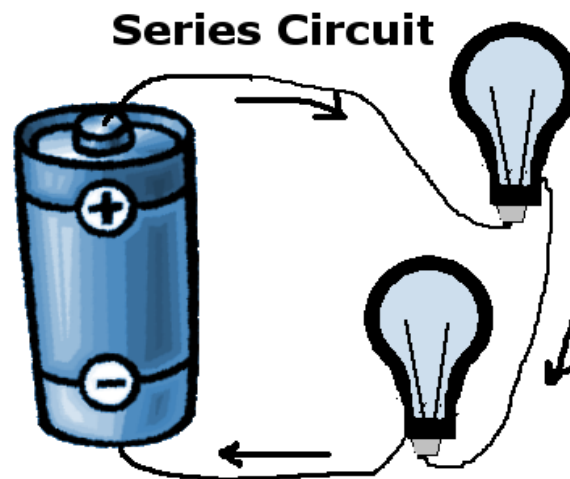


¥ Schematic Diagram of a Simple Circuit

The following is a schematic diagram of the simple circuit showing the electronic symbols for the battery, switch, and bulb.

Schematic Diagram of a Simple Circuit

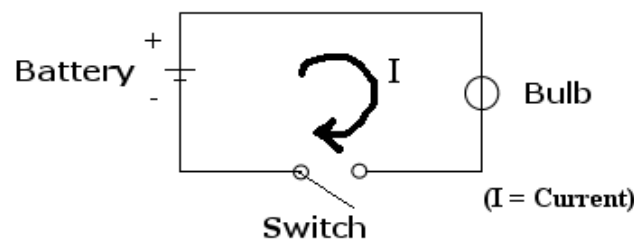

Electric Switches

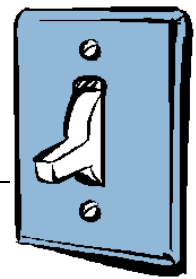


Student Resource: Simulating a Switch


¥ Simulating a Switch by Disconnecting a Wire

You can make a crude switch just by disconnecting one of the wires and alternately touching it and removing it from the metal case of the bulb. Why does the light go off when the wire is no longer touching? When the wire is removed, the electrons would have to flow through the air in order to complete the circuit. To make electrons flow through air requires a lot more energy than is available, because nearly all the electrons in the air are tightly bound to atoms. The same is true of all the other materials known as insulators. The makeshift switch that is made by disconnecting and reconnecting the wire does exactly the same thing as a manufactured switch, except that manufactured ones are more reliable. All they do is disconnect and reconnect the wires when you move the lever, push the button, turn the knob, or slide the button.

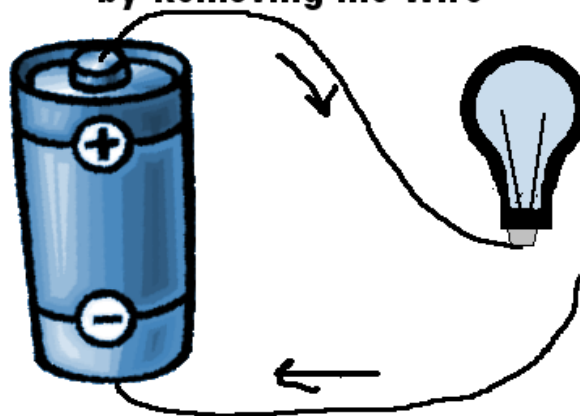Simulating a Simple Switch by Removing the Wire




Schematic Diagram of a Simple Circuit

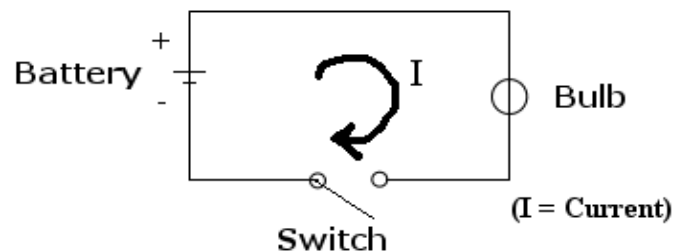

Electric Switches

Electric Switches

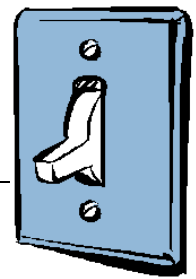

Student Worksheet: Identifying Switches in the Home

¥ Challenge


Describe the function of switches on the following household appliances. Is there more than one switch on any of these items?



Portable Vacuum



Toaster

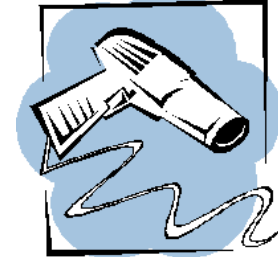


Hair Dryer



Coffee Maker




Electric Fan

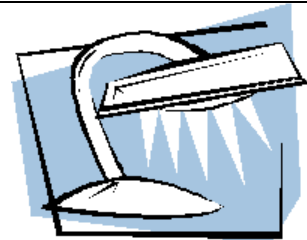

Desk Lamp

Electric Switches

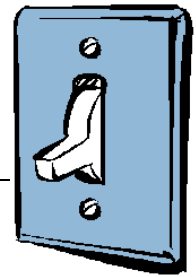

Student Worksheet:

¥ You are the Engineer!

Instructions:

1. You need to design a system that will turn a light on and off in the hallway of a new office building.
2. Build a working circuit with just a battery and a bulb.
3. Next, add a switch in such a way that the switch turns the bulb on and off.
4. Draw and describe your circuits and switches in the space below using the schematic symbols shown on the Student Resource Sheet.
5. Discuss your designs and experiences with the class.

Circuit Without Switch	Circuit With Switch

¥ Describe what you did to make the bulb light up using the switch:

¥ What materials did you use to make your own switch?